


Event-B Course

8. Electronic Circuit Development


Jean-Raymond Abrial

September-October-November 2011

 
- To present a methodology for developing electronic circuits
- To cover the development of three examples




 
- It is made of the following components:
 - two **input wires** *i1* and *i2* carrying boolean values,
 - two **output wires** *o1* and *o2* carrying boolean values,
 - various **gates** (here three and-gates and two not-gates),
 - a **register** *p2* containing a boolean value.





 
- Initially: $p2 = \text{TRUE}$
 $i1 = \text{TRUE}$
 $i2 = \text{TRUE}$




 


 


 


  



 


 

 


 

 


  


- A Circuit

 

- A Clock

 

 - When the clock is *low*:
 - *cir_state* and the *output* wires are supposed to stay idle
 - only the *input* wires may be modified,
- When the clock is *high*:
 - the *input* wires are supposed to stay idle
 - *cir_state* and *output* wires may be modified.
- *cir_state* and *output* form the circuit
- *input* and also outside state *env_state* form the environment



The notion of clock can be made more abstract.

- Two alternative ways of **observing the closed system**.
- Here are these two **modes** of observation:
 - ***env***, corresponds to observing the environment,
 - ***cir***, consists in observing the circuit.

Such modes **alternate for ever**.

- Let c be the **circuit** variables and e be the **environment** variables

- Circuit Events

```
cir_event_i
  when
    mode = cir
     $GC\_i(input, c)$ 
  then
    mode := env
     $c, output :| PC\_i(input, c, c', output')$ 
  end
```

- Environment Events

```
env_event_j
  when
    mode = env
     $GE\_j(output, e)$ 
  then
    mode := cir
     $e, input :| PE\_j(output, e, e', input')$ 
  end
```

- The **final circuit**:
 - uses the *input*
 - modifies *c* and *output*
 - never accesses *e*
- The **final environment**:
 - uses the *output*
 - modifies *e* and *input*
 - never accesses *c*
- Warning: **this is not necessary the case before last refinement**

$$mode = env \Rightarrow C(e, input, c, output)$$

$$mode = cir \Rightarrow D(e, input, c, output)$$

- C states what the circuit establishes for the environment provided the circuit behaves in a situation where D holds.
- D states what the environment establishes for the circuit provided the environment behaves in a situation where C holds.

$$\begin{array}{l} C(e, input, c, output) \\ GE_j(output, e) \\ PE_j(output, e, e', input') \\ \Rightarrow \\ D(e', input', c, output) \end{array}$$

$$\begin{array}{l} D(e, input, c, output) \\ GC_i(input, c) \\ PC_i(input, c, c', output') \\ \Rightarrow \\ C(e, input, c', output') \end{array}$$

- When C holds, then D must hold after any modifications e' and $input'$ made by the environment.
- When D holds, then C must hold after any modifications c' and $output'$ made by the circuit.

- the **circuit** variables must all be **boolean**,
- the **inputs** must be **boolean**,
- the **outputs** must be **boolean**,
- the **circuit** must be **deadlock free**,

- the circuit must be **internally deterministic** (variable assignments),
- the circuit must be **externally deterministic** (guards),
- the **environment does not access the circuit variables**,
- the **circuit does not access the environment variables**.

```
cir_event_i
  when
    mode = cir
    GC_i(input, c)
  then
    mode := env
    c := C_i(input, c)
    output := O_i(input, c)
  end
```

- Deadlock Freeness: Disjunction of guards

$$mode = cir \Rightarrow GC_1(input, c) \vee \dots \vee GC_n(input, c)$$

- External Determinacy: Mutual exclusion of guards

$$mode = cir \Rightarrow \neg (GC_i(input, c) \wedge GC_j(input, c))$$

```
cir_event_i
  when
    mode = cir
    GC_i(input, c)
  then
    mode := env
    c := bool  $\left( \begin{array}{c} \dots \vee \\ GC\_i(input, c) \wedge C\_i(input, c) = \text{TRUE} \vee \\ \dots \end{array} \right)$ 
    output := bool  $\left( \begin{array}{c} \dots \vee \\ GC\_i(input, c) \wedge O\_i(input, c) = \text{TRUE} \vee \\ \dots \end{array} \right)$ 
  end
```

The **bool** operator: transforming a **predicate** into a **boolean expression**

$$E = \text{bool}(P) \Leftrightarrow \left(\begin{array}{l} P \Rightarrow E = \text{TRUE} \\ \neg P \Rightarrow E = \text{FALSE} \end{array} \right)$$

```
(abstract_)cir_event_i
  when
    mode = cir
    GC_i(input, c)
  then
    mode := env
    c := C_i(input, c)
    output := O_i(input, c)
  end
```

```
(concrete_)cir_event_i
  when
    mode = cir
    GC_i(input, c)
  then
    mode := env
    c := bool  $\left( \begin{array}{c} \dots \vee \\ GC_i(input, c) \wedge C_i(input, c) = \text{TRUE} \vee \\ \dots \end{array} \right)$ 
    output := bool  $\left( \begin{array}{c} \dots \vee \\ GC_i(input, c) \wedge O_i(input, c) = \text{TRUE} \vee \\ \dots \end{array} \right)$ 
  end
```

$$\begin{aligned}
 & GC_i(input, c) \\
 \Rightarrow & \\
 & C_i(input, c) = \text{bool} \left(\begin{array}{c} \dots \vee \\ GC_i(input, c) \wedge C_i(input, c) = \text{TRUE} \vee \\ \dots \end{array} \right)
 \end{aligned}$$

- According to the definition of `bool`, this reduces to the following two statements:

$$\begin{aligned}
 & GC_i(input, c) \\
 & \left(\begin{array}{c} \dots \vee \\ GC_i(input, c) \wedge C_i(input, c) = \text{TRUE} \vee \\ \dots \end{array} \right) \\
 \Rightarrow & \\
 & C_i(input, c) = \text{TRUE} \\
 \\
 & GC_i(input, c) \\
 & \neg \left(\begin{array}{c} \dots \vee \\ GC_i(input, c) \wedge C_i(input, c) = \text{TRUE} \vee \\ \dots \end{array} \right) \\
 \Rightarrow & \\
 & C_i(input, c) = \text{FALSE}
 \end{aligned}$$

$$\begin{array}{l} GC_i(input, c) \\ \left(\begin{array}{c} \dots \vee \\ GC_i(input, c) \wedge C_i(input, c) = \text{TRUE} \vee \\ \dots \end{array} \right) \\ \Rightarrow \\ C_i(input, c) = \text{TRUE} \end{array}$$

- Since the guard are mutually exclusive, it can be reduced to:

$$\begin{array}{l} GC_i(input, c) \\ C_i(input, c) = \text{TRUE} \\ \Rightarrow \\ C_i(input, c) = \text{TRUE} \end{array}$$

$$\neg \left(\begin{array}{c} GC_i(input, c) \\ \vdots \vee \\ GC_i(input, c) \wedge C_i(input, c) = \text{TRUE} \vee \\ \vdots \end{array} \right) \Rightarrow C_i(input, c) = \text{FALSE}$$

- Equivalently:

$$\begin{array}{c} GC_i(input, c) \\ \vdots \\ (\neg GC_i(input, c) \vee C_i(input, c) = \text{FALSE}) \\ \vdots \\ \Rightarrow C_i(input, c) = \text{FALSE} \end{array}$$

- Reducing to:

$$\begin{array}{c} GC_i(input, c) \\ \vdots \\ C_i(input, c) = \text{FALSE} \\ \vdots \\ \Rightarrow C_i(input, c) = \text{FALSE} \end{array}$$

- The circuit events are **deadlock free** (disjunction of guards holds)
- They have **identical actions**,
- They can all be **merged into a single event** as follows:

```

circuit_event
  when
    mode = cir
  then
    mode := env
    c := bool  $\left( \begin{array}{c} \dots \vee \\ GC\_i(input, c) \wedge C\_i(input, c) = \text{TRUE} \vee \\ \dots \end{array} \right)$ 
    output := bool  $\left( \begin{array}{c} \dots \vee \\ GC\_i(input, c) \wedge O\_i(input, c) = \text{TRUE} \vee \\ \dots \end{array} \right)$ 
  end
    
```

- **Merging** consists of making a **single circuit** with **several** having the **same actions**:
 - **disjunction of guards** (here TRUE because of deadlock freeness)
 - **same identical action**

- When $C_i(input, c)$ is syntactically equal to **TRUE** then $C_i(input, c) = \text{TRUE}$ can be removed,

```
circuit_event
  when
    mode = cir
  then
    mode := env
    c := bool  $\left( \begin{array}{c} \dots \vee \\ GC\_i(input, c) \wedge \text{TRUE} = \text{TRUE} \vee \\ \dots \end{array} \right)$ 
    output := bool  $\left( \begin{array}{c} \dots \vee \\ GC\_i(input, c) \wedge O\_i(input, c) = \text{TRUE} \vee \\ \dots \end{array} \right)$ 
  end
```

- Same for $O_i(input, c)$

- When $C_i(input, c)$ is syntactically equal to FALSE then $GC_i(input, c) \wedge C_i(input, c) = \text{TRUE}$ can be removed.

```

circuit_event
  when
    mode = cir
  then
    mode := env
    c := bool  $\left( \begin{array}{c} \dots \vee \\ GC\_i(input, c) \wedge \text{FALSE} = \text{TRUE} \vee \\ \dots \end{array} \right)$ 
    output := bool  $\left( \begin{array}{c} \dots \vee \\ GC\_i(input, c) \wedge O\_i(input, c) = \text{TRUE} \vee \\ \dots \end{array} \right)$ 
  end

```

- Same for $O_i(input, c)$

set: $MODE$

constants: env
 cir

axm_1: $\text{partition}(MODE, \{env\}, \{cir\})$

variables: $input1$
 $input2$
 $output$

inv0_1: $input1 \in \text{BOOL}$

inv0_2: $input2 \in \text{BOOL}$

inv0_3: $output \in \text{BOOL}$

```
env1
  when
    mode = env
  then
    mode := cir
    input1 :∈ BOOL
    input2 :∈ BOOL
  end
```

cir1

when

mode = *cir*

input_1 = TRUE

input_2 = TRUE

then

mode := *env*

output := TRUE

end

cir2

when

mode = *cir*

input_1 = TRUE

input_2 = FALSE

then

mode := *env*

output := TRUE

end

cir3

when

mode = *cir*

input_1 = FALSE

input_2 = TRUE

then

mode := *env*

output := TRUE

end

cir4

when

mode = *cir*

input_1 = FALSE

input_2 = FALSE

then

mode := *env*

output := FALSE

end

- the **circuit** variables must all be **boolean**,
- the **inputs** must be **boolean**,
- the **outputs** must be **boolean**,
- the **circuit** must be deadlock free,

- the circuit must be **internally deterministic** (variable assignments),
- the circuit must be **externally deterministic** (guards),
- the **environment does not access the circuit variables**,
- the **circuit does not access the environment variables**.


```

cir1
  when
    mode = cir
    input_1 = TRUE
    input_2 = TRUE
  then
    mode := env
    output := TRUE
  end
    
```

```

cir2
  when
    mode = cir
    input_1 = TRUE
    input_2 = FALSE
  then
    mode := env
    output := TRUE
  end
    
```

```

cir3
  when
    mode = cir
    input_1 = FALSE
    input_2 = TRUE
  then
    mode := env
    output := TRUE
  end
    
```

```

cir4
  when
    mode = cir
    input_1 = FALSE
    input_2 = FALSE
  then
    mode := env
    output := FALSE
  end
    
```


$$\text{bool} \left(\begin{array}{l} (input_1 = \text{TRUE} \wedge input_2 = \text{TRUE} \wedge \text{TRUE} = \text{TRUE}) \vee \\ (input_1 = \text{TRUE} \wedge input_2 = \text{FALSE} \wedge \text{TRUE} = \text{TRUE}) \vee \\ (input_1 = \text{FALSE} \wedge input_2 = \text{TRUE} \wedge \text{TRUE} = \text{TRUE}) \vee \\ (input_1 = \text{FALSE} \wedge input_2 = \text{FALSE} \wedge \text{FALSE} = \text{TRUE}) \end{array} \right)$$

$$\text{bool} \left(\begin{array}{l} (input_1 = \text{TRUE} \wedge input_2 = \text{TRUE} \wedge \text{TRUE} = \text{TRUE}) \vee \\ (input_1 = \text{TRUE} \wedge input_2 = \text{FALSE} \wedge \text{TRUE} = \text{TRUE}) \vee \\ (input_1 = \text{FALSE} \wedge input_2 = \text{TRUE} \wedge \text{TRUE} = \text{TRUE}) \vee \\ (input_1 = \text{FALSE} \wedge input_2 = \text{FALSE} \wedge \text{FALSE} = \text{TRUE}) \end{array} \right)$$


reducing to:

$$\text{bool}(input_1 = \text{TRUE} \vee input_2 = \text{TRUE})$$
 
```
or_gate
  refines
    cir1
    cir2
    cir3
    cir4
  when
    mode = cir
  then
    mode := env
    output := bool(input_1 = TRUE ∨ input_2 = TRUE)
  end
```



 - The lamp must **flash once** between button **depression** and subsequent **release**.



- The flash may occur **very early**: just after button depression
- or in **between** button **depression** and subsequent **release**
- or **very late**: just after button release
- We have a certain **non-determinacy**

set: $MODE$

constants: env
 cir

axm_1: $\text{partition}(MODE, \{env\}, \{cir\})$

- *push*: number of times the button is depressed
- *pop*: number of times the button is released

variables: $mode, push, pop$

inv0_1: $mode \in MODE$

inv0_2: $push \in \mathbb{N}$

inv0_3: $pop \in \mathbb{N}$

inv0_4: $pop \leq push$

inv0_5: $push \leq pop + 1$

In other words:

$$push \in \{pop, pop + 1\}$$

- *flash*: number of times the lamp *flashes*

variables: $\dots, flash$

inv0_6: $flash \in \mathbb{N}$

inv0_7: $flash \leq push$

inv0_8: $push \leq flash + 1$

- In other words:

$$push \in \{flash, flash + 1\}$$

env1

when

mode = env

pop = push

then

mode := cir

push := push + 1

end

env2

when

mode = env

pop ≠ push

then

mode := cir

pop := pop + 1

end

env3

when

mode = env

then

mode := cir

end

init

mode := env


push := 0

pop := 0


flash := 0


```
cir1
  when
    mode = cir
    push  $\neq$  flash
  then
    mode := env
    flash := flash + 1
  end
```


- Button has been depressed and **flash not done yet**
- Notice that button **might have been just released** (*push* = *pop*)

 


Case 1

 


Case 2

 


Case 1

 


Case 1

 


Case 2

 


Case 3

 

Case 1

 

Case 2

 


Case 3


Condition *A*: $push = pop \wedge push = flash$

Condition *B*: $push \neq pop \wedge push \neq flash$


Condition *C*: $push \neq pop \wedge push = flash$

 

Case 1

 

Case 2

 

Case 3

Condition *A*: $push = pop \wedge push = flash$

Condition *B*: $push \neq pop \wedge push \neq flash$

Condition *C*: $push \neq pop \wedge push = flash$

- Guard of "do-nothing":

$$A \vee B \vee C \Leftrightarrow push \neq pop \vee push = flash$$

```
cir2
  when
     $mode = cir$ 
     $push \neq pop \vee push = flash$ 
  then
     $mode := env$ 
  end
```

- We cannot prove that the event `env1` preserves invariant `inv0_8`

```
env1
  when
    mode = env
    pop = push
  then
    mode := cir
    push := push + 1
  end
```

inv0_7: $flash \leq push$

inv0_8: $push \leq flash + 1$

- The following invariant has to be added:

inv0_9: $mode = env \wedge pop = push \Rightarrow push + 1 \leq flash + 1$

- That is (according to **inv0_7**):

inv0_9: $mode = env \wedge pop = push \Rightarrow push = flash$

```
cir1
  when
    mode = cir
    push ≠ flash
  then
    mode := env
    flash := flash + 1
  end
```

```
cir2
  when
    mode = cir
    push ≠ pop ∨ push = flash
  then
    mode := env
  end
```

- The guard are **both true** when *push ≠ flash* and *push ≠ pop* both hold
 - When the flash has not yet occurred (*push ≠ flash*)
 - When we are in between a depression and release (*push ≠ pop*)
- We can either **flash** (cir1) or **do nothing** (cir2)


```
cir1
  when
    mode = cir
    push  $\neq$  flash
  then
    mode := env
    flash := flash + 1
  end
```

```
cir2
  when
    mode = cir
    push  $\neq$  pop  $\vee$  push = flash
  then
    mode := env
  end
```

- Two solutions:
 - removing *push $\neq$ pop* in cir2
 - adding *push = pop* in cir1
- First solution: flashing as **early** as possible
- Second solution: flashing as **late** as possible

cir1_PULSER1

when

$mode = cir$

$push \neq flash$

then

$mode := env$

$flash := flash + 1$

end

cir2_PULSER1

when

$mode = cir$

$push = flash$

then

$mode := env$

end

- **Early flash**: as soon as $push$ is different from $flash$
(just after depressing the button)

cir1_PULSER2

when

$mode = cir$

$push = pop \wedge push \neq flash$

then

$mode := env$

$flash := flash + 1$

end

cir2_PULSER2

when

$mode = cir$

$push \neq pop \vee push = flash$

then

$mode := env$

end

- **Late flash**: both $push$ and pop are the same
- Button release has occurred
- But the $flash$ has not yet occurred

- Introducing boolean Input and Output

variables: $mode, input, output$

inv2_1: $input \in \text{BOOL}$

inv2_2: $output \in \text{BOOL}$

```
(abstract-)env1
  when
    mode = env
    pop = push
  then
    mode := cir
    push := push + 1
  end
```

```
(abstract-)env2
  when
    mode = env
    pop ≠ push
  then
    mode := cir
    pop := pop + 1
  end
```

```
(abstract-)env3
  when
    mode = env
  then
    mode := cir
  end
```

```
env1
  when
    mode = env
    input = FALSE
  then
    mode := cir
    input := TRUE
  end
```

```
env2
  when
    mode = env
    input = TRUE
  then
    mode := cir
    input := FALSE
  end
```

```
env3
  when
    mode = env
  then
    mode := cir
  end
```

inv2_3: $input = \text{TRUE} \Leftrightarrow pop \neq push$

```
(abstract-)cir1_PULSER1
  when
    mode = cir
    push ≠ flash
  then
    mode := env
    flash := flash + 1
  end
```

```
(abstract-)cir2_PULSER1
  when
    mode = cir
    push = flash
  then
    mode := env
  end
```

```
variables: ..., reg
```

```
inv2_4:   reg ∈ BOOL
```

```
invi2_5:  mode = env ⇒ reg = input
```

- Variable *reg* records the previous value of *input*

```
cir1_PULSER1
  when
    mode = cir
    input = TRUE ∧ reg = FALSE
    /* push just changed */
  then
    mode := env
    output := TRUE
    reg := input
  end
```

```
cir2_PULSER1
  when
    mode = cir
    input = FALSE ∨ reg = TRUE
  then
    mode := env
    output := FALSE
    reg := input
  end
```

```
(abstract-)cir1_PULSER1
  when
    mode = cir
    push ≠ flash
  then
    mode := env
    flash := flash + 1
  end
```

```
(abstract-)cir2_PULSER1
  when
    mode = cir
    push = flash
  then
    mode := env
  end
```

```
cir1_PULSER1
  when
    mode = cir
    input = TRUE ∧ reg = FALSE
  then
    mode := env
    output := TRUE
    reg := input
  end
```

```
cir2_PULSER1
  when
    mode = cir
    input = FALSE ∨ reg = TRUE
  then
    mode := env
    output := FALSE
    reg := input
  end
```

inv2_PULSER1_6: $mode = cir \Rightarrow \left(\begin{array}{l} input = TRUE \wedge reg = FALSE \\ \Leftrightarrow \\ push \neq flash \end{array} \right)$

(abstract-)cir1_PULSER2

```

when
  mode = cir
  push = pop  $\wedge$  push  $\neq$  flash
then
  mode := env
  flash := flash + 1
end

```

(abstract-)cir2_PULSER2

```

when
  mode = cir
  push  $\neq$  pop  $\vee$  push = flash
then
  mode := env
end

```

cir1_PULSER2

```

when
  mode = cir
  input = FALSE  $\wedge$  reg = TRUE
  /* pop just changed */
then
  mode := env
  output := TRUE
  reg := input
end

```

cir2_PULSER2

```

when
  mode = cir
  input = TRUE  $\vee$  reg = FALSE
then
  mode := env
  output := FALSE
  reg := input
end

```

inv2_PULSER2_6: $mode = cir \Rightarrow \left(\begin{array}{l} input = FALSE \wedge reg = TRUE \\ \Leftrightarrow \\ push \neq flash \wedge push = pop \end{array} \right)$

- the **circuit** variables must all be **boolean**,
- the **inputs** must be **boolean**,
- the **outputs** must be **boolean**,
- the **circuit** must be **deadlock free**,

-
- the circuit must be **internally deterministic** (variable assignments),
 - the circuit must be **externally deterministic** (guards),
 - the **environment does not access the circuit variables**,
 - the **circuit does not access the environment variables**.

cir1_PULSER1

when

mode = *cir*

input = TRUE $\wedge$ *reg* = FALSE

then

mode := *env*

output := TRUE

reg := *input*

end

cir2_PULSER1

when

mode = *cir*

input = FALSE $\vee$ *reg* = TRUE

then

mode := *env*

output := FALSE

reg := *input*

end

PULSER1

when

mode = *cir*

then

mode := *env*

output := bool($((input = \text{TRUE} \wedge reg = \text{FALSE} \wedge \text{TRUE} = \text{TRUE}) \vee$
 $((input = \text{FALSE} \vee reg = \text{TRUE}) \wedge \text{FALSE} = \text{TRUE}))$)

reg := bool($((input = \text{TRUE} \wedge reg = \text{FALSE} \wedge input = \text{TRUE}) \vee$
 $((input = \text{FALSE} \vee reg = \text{TRUE}) \wedge input = \text{TRUE}))$)

end

PULSER1

when

mode = cir


then

mode := env

output := bool(input = TRUE $\wedge$ reg = FALSE)

reg := bool(input = TRUE)

end

 

cir1_PULSER2

when

mode = *cir*

input = FALSE $\wedge$ *reg* = TRUE

then

mode := *env*

output := TRUE

reg := *input*

end

cir2_PULSER2

when

mode = *cir*

input = TRUE $\vee$ *reg* = FALSE

then

mode := *env*

output := FALSE

reg := *input*

end

PULSER2

when

mode = *cir*

then

mode := *env*

output := bool($((input = \text{FALSE} \wedge reg = \text{TRUE} \wedge \text{TRUE} = \text{TRUE}) \vee$
 $((input = \text{TRUE} \vee reg = \text{FALSE}) \wedge \text{FALSE} = \text{TRUE}))$)

reg := bool($((input = \text{FALSE} \wedge reg = \text{TRUE} \wedge input = \text{TRUE}) \vee$
 $((input = \text{TRUE} \vee reg = \text{FALSE}) \wedge input = \text{TRUE}))$)

end

PULSER2

when

mode = *cir*


then

mode := *env*


output := bool(*input* = FALSE $\wedge$ *reg* = TRUE)

reg := bool(*input* = TRUE)


end

 



- Pulser1

 



- Pulser2

 


 


 


 


 


 


 


 


 


 


 


 


 


 


 


 


 


 


 


 


 


 


 


 


 

 

 

 

 



The circuit has two boolean inputs *i1* and *i2* and two boolean outputs *o1* and *o2*

FUN-1

A **TRUE** input means a user, associated with that input, is asking for a certain resource

FUN-2

The circuit reacts positively to a request by setting the corresponding output to **TRUE**

FUN-3

The circuit can react positively to **one request only at a time** (mutual exclusion)

FUN-4

Each user frees the resource immediately

FUN-5

A requesting user **cannot be postponed indefinitely**

FUN-6

A user asking for a resource continues to ask for it as long as it is not served

FUN-7

The resource cannot be granted without a user asking for it

FUN-8



- r_i denotes the number of requests made by user i
- a_i denotes the number of acknowledgements made by the circuit for user i

- ri number of requests made so far by user i
- ai number of acknowledgements made so far for user i

variables: $r1, r2, a1, a2$

inv0_1: $r1 \in \mathbb{N}$

inv0_2: $r2 \in \mathbb{N}$

inv0_3: $a1 \in \mathbb{N}$

inv0_4: $a2 \in \mathbb{N}$

$$\mathbf{inv0_5:} \quad a1 \leq r1$$

$$\mathbf{inv0_6:} \quad r1 \leq a1 + 1$$

$$\mathbf{inv0_7:} \quad a2 \leq r2$$

$$\mathbf{inv0_8:} \quad r2 \leq a2 + 1$$

- Number of requests greater or equal to the number of acks.
(no spurious acks)
- The number of requests never exceeds the number of ack.
by more than 1 (users never quit without being served)

- A requesting user never starves

variables: $p1, p2$

- $pi = \text{TRUE}$ means user i waits to be served

inv0_9: $p1 \in \text{BOOL}$

inv0_10: $p2 \in \text{BOOL}$

inv0_11: $p1 = \text{FALSE} \vee p2 = \text{FALSE}$

inv0_12: $mode = env \Rightarrow (r1 = a1 \Leftrightarrow p1 = \text{FALSE})$

inv0_13: $mode = env \Rightarrow (r2 = a2 \Leftrightarrow p2 = \text{FALSE})$

- Asking for user 1 or for user 2

```
env1
  when
    mode = env
    r1 = a1
  then
    mode := cir
    r1 := r1 + 1
  end
```

```
env2
  when
    mode = env
    r2 = a2
  then
    mode := cir
    r2 := r2 + 1
  end
```

- Asking for both users

```
env3
  when
    mode = env
    r1 = a1
    r2 = a2
  then
    mode := cir
    r1 := r1 + 1
    r2 := r2 + 1
  end
```

```
env0
  when
    mode = env
  then
    mode := cir
  end
```

- Note the last "do-nothing" event

cir1

when $mode = cir$ $r1 \neq a1$ $p2 = \text{FALSE}$ **then** $mode := env$ $a1 := a1 + 1$ $p1 := \text{FALSE}$ $p2 := \text{bool}(r2 \neq a2)$ **end**

cir2

when $mode = cir$ $r2 \neq a2$ $p1 = \text{FALSE}$ **then** $mode := env$ $a2 := a2 + 1$ $p2 := \text{FALSE}$ $p1 := \text{bool}(r1 \neq a1)$ **end**

- Notice the external non-determinacy

- A circuit "do-nothing" event

```
cir0
  when
    mode = cir
    r1 = a1
    r2 = a2
  then
    mode := env
    p1 := FALSE
    p2 := FALSE
  end
```

$$mode = cir \Rightarrow \left(\begin{array}{l} r1 \neq a1 \wedge p2 = \text{FALSE} \vee \\ r2 \neq a2 \wedge p1 = \text{FALSE} \vee \\ r1 = a1 \wedge r2 = a2 \end{array} \right)$$

We have to add the following invariants:

inv0_14: $mode = cir \Rightarrow (r1 = a1 \Rightarrow p1 = \text{FALSE})$

inv0_15: $mode = cir \Rightarrow (r2 = a2 \Rightarrow p2 = \text{FALSE})$

- 53 proofs
- All automatic

- Inputs $r1$ and $r2$ are not boolean
- Outputs $a1$ and $a2$ are not boolean
- Circuit reads its outputs $a1$ and $a2$
- Circuit is externally non-deterministic

- Delivering boolean outputs $o1$ and $o2$ (the offsets to $a1$ and $a2$)
- Pushing $a1$ and $a2$ outside of the circuit: $b1$ and $b2$
- $b1$ and $b2$ are slightly shifted

variables: $b1, o1,$
 $b2, o2$

inv1_1: $b1 \in \mathbb{N}$

inv1_2: $o1 \in \text{BOOL}$

inv1_3: $b2 \in \mathbb{N}$

inv1_4: $o2 \in \text{BOOL}$

- Transforming a boolean into a number (0 or 1)

constants: b_2_01

prp1_1: $b_2_01 \in \text{BOOL} \rightarrow \{0, 1\}$

prp1_2: $b_2_01(\text{TRUE}) = 1$

prp1_3: $b_2_01(\text{FALSE}) = 0$

inv1_5: $mode = cir \Rightarrow a1 = b1$

inv1_6: $mode = cir \Rightarrow a2 = b2$

inv1_7: $mode = env \Rightarrow a1 = b1 + b_2_01(o1)$

inv1_8: $mode = env \Rightarrow a2 = b2 + b_2_01(o2)$

env1

when

$mode = env$

$r1 = b1 + b_2_01(o1)$

then

$mode := cir$

$r1 := r1 + 1$

$b1 := b1 + b_2_01(o1)$

$b2 := b2 + b_2_01(o2)$

end

env2

when

$mode = env$

$r2 = b2 + b_2_01(o2)$

then

$mode := cir$

$r2 := r2 + 1$

$b1 := b1 + b_2_01(o1)$

$b2 := b2 + b_2_01(o2)$

end

```
env3
  when
    mode = env
    r1 = b1 + b_2_01(o1)
    r2 = b2 + b_2_01(o2)
  then
    mode := cir
    r1 := r1 + 1
    r2 := r2 + 1
    b1 := b1 + b_2_01(o1)
    b2 := b2 + b_2_01(o2)
  end
```

```
(abstract-)env3
  when
    mode = env
    r1 = a1
    r2 = a2
  then
    mode := cir
    r1 := r1 + 1
    r2 := r2 + 1
  end
```

inv1_7: $mode = env \Rightarrow a1 = b1 + b_2_01(o1)$

inv1_8: $mode = env \Rightarrow a2 = b2 + b_2_01(o2)$

```
cir1
  when
    mode = cir
    r1 ≠ b1
    p2 = FALSE
  then
    mode := env
    o1 := TRUE
    o2 := FALSE
    p1 := FALSE
    p2 := bool(r2 ≠ b2)
  end
```

```
(abstract-)cir1
  when
    mode = cir
    r1 ≠ a1
    p2 = FALSE
  then
    mode := env
    a1 := a1 + 1
    p1 := FALSE
    p2 := bool(r2 ≠ a2)
  end
```

inv1_5: $mode = cir \Rightarrow a1 = b1$

inv1_6: $mode = cir \Rightarrow a2 = b2$

cir2

when

$mode = cir$

$r2 \neq b2$

$p1 = \text{FALSE}$

then

$mode := env$

$o1 := \text{FALSE}$

$o2 := \text{TRUE}$

$p1 := \text{bool}(r1 \neq b1)$

$p2 := \text{FALSE}$

end

cir0

when

$mode = cir$

$r1 = b1$

$r2 = b2$

then

$mode := env$

$o1 := \text{FALSE}$

$o2 := \text{FALSE}$

$p1 := \text{FALSE}$

$p2 := \text{FALSE}$

end

- 57 Proofs
- all automatic

- Inputs are not boolean: $r1$ and $r2$
- Circuit is accessing environment variables: $b1$ and $b2$
- Circuit still externally non-deterministic

- Introducing boolean inputs $i1$ and $i2$.

variables: $i1, i2$

inv2_1: $i1 \in \text{BOOL}$

inv2_2: $i2 \in \text{BOOL}$

- Gluing Invariant:

inv2_2: $mode = cir \Rightarrow (i1 = \text{FALSE} \Leftrightarrow r1 = b1)$

inv2_3: $mode = cir \Rightarrow (i2 = \text{FALSE} \Leftrightarrow r2 = b2)$

```
cir1
  when
    mode = cir
    i1 = TRUE
    p2 = FALSE
  then
    mode := env
    o1 := TRUE
    o2 := FALSE
    p1 := FALSE
    p2 := i2
  end
```

```
(abstract-)cir1
  when
    mode = cir
    r1 ≠ b1
    p2 = FALSE
  then
    mode := env
    o1 := TRUE
    o2 := FALSE
    p1 := FALSE
    p2 := bool(r2 ≠ b2)
  end
```

inv2_2: $mode = cir \Rightarrow (i1 = \text{FALSE} \Leftrightarrow r1 = b1)$

inv2_3: $mode = cir \Rightarrow (i2 = \text{FALSE} \Leftrightarrow r2 = b2)$

cir2

when

mode = *cir*

i2 = TRUE

p1 = FALSE

then

mode := *env*

o1 := FALSE

o2 := TRUE

p1 := *i1*

p2 := FALSE

end

cir0

when

mode = *cir*

i1 = FALSE

i2 = FALSE

then

mode := *env*

o1 := FALSE

o2 := FALSE

p1 := FALSE

p2 := FALSE

end

- 26 Proofs
- All automatic

- Circuit still non-deterministic

- Removing variables $p1$

```
cir1
  when
    mode = cir
    i1 = TRUE
    p2 = FALSE
  then
    mode := env
    o1 := TRUE
    o2 := FALSE
    p2 := i2
  end
```

```
cir2
  when
    mode = cir
    i2 = TRUE
     $\neg (i1 = \text{TRUE} \wedge p2 = \text{FALSE})$ 
  then
    mode := env
    o1 := FALSE
    o2 := TRUE
    p2 := FALSE
  end
```



```
cir0
  when
    mode = cir
    i1 = FALSE
    i2 = FALSE
  then
    mode := env
    o1 := FALSE
    o2 := FALSE
    p2 := FALSE
  end
```

$$\begin{array}{l} \text{thm3_1:} \quad \text{mode} = \text{cir} \\ \Rightarrow \\ \left(\begin{array}{l} i1 = \text{TRUE} \wedge p2 = \text{FALSE} \\ i2 = \text{TRUE} \wedge \neg(i1 = \text{TRUE} \wedge p2 = \text{FALSE}) \\ i1 = \text{FALSE} \wedge i2 = \text{FALSE} \end{array} \vee \right) \end{array}$$

- Note that the circuit is now clearly deterministic

- 5 proofs
- All automatic
- Total: 136 proofs


```
cir1
  when
    mode = cir
    i1 = TRUE
    p2 = FALSE
  then
    mode := env
    o1 := TRUE
    o2 := FALSE
    p2 := i2
  end
```

```
cir2
  when
    mode = cir
    i2 = TRUE
     $\neg \left( \begin{array}{l} i1 = \text{TRUE} \\ p2 = \text{FALSE} \end{array} \right)$ 
  then
    mode := env
    o1 := FALSE
    o2 := TRUE
    p2 := FALSE
  end
```


```
cir0
  when
    mode = cir
    i1 = FALSE
    i2 = FALSE
  then
    mode := env
    o1 := FALSE
    o2 := FALSE
    p2 := FALSE
  end
```

```
arbiter
  when
    mode = cir
  then
    mode := env
    o1 := bool ( i1 = TRUE  $\wedge$  p2 = FALSE )
    o2 := bool ( i2 = TRUE  $\wedge$   $\neg$  ( i1 = TRUE  $\wedge$  p2 = FALSE ) )
    p2 := bool ( i1 = TRUE  $\wedge$  p2 = FALSE  $\wedge$  i2 = TRUE )
  end
```
 
```
arbiter
  when
    mode = cir
  then
    mode := env
    o1 := bool ( i1 = TRUE  ∧  p2 = FALSE )
    o2 := bool ( i2 = TRUE  ∧  ¬ ( i1 = TRUE  ∧  p2 = FALSE ) )
    p2 := bool ( i1 = TRUE  ∧  p2 = FALSE  ∧  i2 = TRUE )
  end
```



 - This example is due to Mead and Conway
- Various traffic lights are situated at the crossing between
 - a small road
 - a main road
- Purpose: to give some priority to the traffic on the main road
- Cars on the small road are detected by appropriate sensors




- **P1**: Main rd. loses priority **when cars are present on the small rd.**
- **P2**: The loss of priority by main rd. occurs **only after a LONG delay**
(even if some cars are present on small road)
- **P3**: Small road loses priority **when there are no cars on it**
- **P4**: Small road also loses priority **after the same LONG delay**
(even if some cars are present on small road)

- **L1:** Traffic lights **transitions** are as usual:
 - green $\rightsquigarrow$ orange
 - orange $\rightsquigarrow$ red
 - red $\rightsquigarrow$ green
- **L2:** An orange light turns red automatically **after a SMALL delay**
- **L3:** When one light is **green or orange**, then **the other is red**

 -
- Rules **P1** to **P4** are dealing with traffic priorities
 - Rules **L1** to **L3** are dealing with traffic lights
 - These questions seem to be independent
 - Making two distinct circuits
 - a Priority circuit
 - a Light circuit
 - Connecting the two circuits





variables: $car, clk,$
 chg, prt

inv0_1: $car \in \text{BOOL}$

inv0_2: $clk \in \text{BOOL}$

inv0_3: $chg \in \text{BOOL}$

inv0_4: $prt \in \text{BOOL}$

- $prt = \text{FALSE}$ means priority on the **main road**
- $prt = \text{TRUE}$ means priority on the **small road**
- $clk = \text{TRUE}$ means long **delay is over**

```
main_to_small
when
    mode = cir
    prt = FALSE
    car = TRUE
    clk = TRUE
then
    mode := env
    prt := TRUE
    chg := TRUE
end
```

- Priority on main road
- Some cars on small road
- Long delay is over

```
small_to_main
  when
    mode = cir
    prt = TRUE
    car = FALSE  $\vee$  clk = TRUE
  then
    mode := env
    prt := FALSE
    chg := TRUE
  end
```

- Priority on small road
- No cars on small road or long delay is over

```
do_nothing_1
  when
    mode = cir
    prt = FALSE
    car = FALSE  $\vee$  clk = FALSE
  then
    mode := env
    chg := FALSE
  end
```

```
do_nothing_2
  when
    mode = cir
    prt = TRUE
    car = TRUE
    clk = FALSE
  then
    mode := env
    chg := FALSE
  end
```

- Priority on main road
- No car on small road or delay is not over
- Priority on small road
- Car on small road
- Delay not over


```
env1
  when
    mode = env
  then
    mode := cir
    car :∈ BOOL
    clk :∈ BOOL
  end
```

$$\begin{array}{l} \text{thm0_1:} \quad \text{mode} = \text{cir} \\ \Rightarrow \\ \left(\begin{array}{l} \text{prt} = \text{FALSE} \wedge \text{car} = \text{TRUE} \wedge \text{clk} = \text{TRUE} \vee \\ \text{prt} = \text{TRUE} \wedge (\text{car} = \text{FALSE} \vee \text{clk} = \text{TRUE}) \vee \\ \text{prt} = \text{FALSE} \wedge (\text{car} = \text{FALSE} \vee \text{clk} = \text{FALSE}) \vee \\ \text{prt} = \text{TRUE} \wedge \text{car} = \text{TRUE} \wedge \text{clk} = \text{FALSE} \end{array} \right) \end{array}$$

- The circuit is deterministic

main_to_small

when

mode = *cir*
prt = FALSE
car = TRUE
clk = TRUE

then

mode := *env*
prt := TRUE
chg := TRUE

end

small_to_main

when

mode = *cir*
prt = TRUE
car = FALSE $\vee$
clk = TRUE

then

mode := *env*
prt := FALSE
chg := TRUE

end

do_nothing_1

when

mode = *cir*
prt = FALSE
car = FALSE $\vee$
clk = FALSE

then

mode := *env*
chg := FALSE
prt := FALSE

end

do_nothing_2

when

mode = *cir*
prt = TRUE
car = TRUE
clk = FALSE

then

mode := *env*
chg := FALSE
prt := TRUE

end

priority

when

mode = *cir*

then

mode := *env*

prt := bool $\left(\begin{array}{l} (prt = \text{FALSE} \wedge car = \text{TRUE} \wedge clk = \text{TRUE}) \vee \\ (prt = \text{TRUE} \wedge car = \text{TRUE} \wedge clk = \text{FALSE}) \end{array} \right)$

chg := bool $\left(\begin{array}{l} (prt = \text{FALSE} \wedge car = \text{TRUE} \wedge clk = \text{TRUE}) \vee \\ (prt = \text{TRUE} \wedge (car = \text{FALSE} \vee clk = \text{TRUE})) \end{array} \right)$

end

```

priority
  when
    mode = cir
  then
    mode := env
    prt := bool  $\left( \begin{array}{l} (prt = \text{FALSE} \wedge car = \text{TRUE} \wedge clk = \text{TRUE}) \vee \\ (prt = \text{TRUE} \wedge car = \text{TRUE} \wedge clk = \text{FALSE}) \end{array} \right)$ 
    chg := bool  $\left( \begin{array}{l} (prt = \text{FALSE} \wedge car = \text{TRUE} \wedge clk = \text{TRUE}) \vee \\ (prt = \text{TRUE} \wedge (car = \text{FALSE} \vee clk = \text{TRUE})) \end{array} \right)$ 
  end
  
```

```

priority
  when
    mode = cir
  then
    mode := env
    prt := bool  $\left( \begin{array}{l} (prt = \text{TRUE} \wedge \neg \left( \begin{array}{l} (car = \text{TRUE} \wedge clk = \text{TRUE}) \vee \\ (car = \text{FALSE} \wedge prt = \text{TRUE}) \end{array} \right) \vee \\ (prt = \text{FALSE} \wedge \left( \begin{array}{l} (car = \text{TRUE} \wedge clk = \text{TRUE}) \vee \\ (car = \text{FALSE} \wedge prt = \text{TRUE}) \end{array} \right) \vee \end{array} \right)$ 
    chg := bool  $\left( \begin{array}{l} (car = \text{TRUE} \wedge clk = \text{TRUE}) \vee \\ (car = \text{FALSE} \wedge prt = \text{TRUE}) \end{array} \right)$ 
  end
  
```

```

priority
  when
    mode = cir
  then
    mode := env
    prt := bool  $\left( (prt = \text{TRUE} \wedge \neg \left( \begin{array}{l} (car = \text{TRUE} \wedge clk = \text{TRUE}) \vee \\ (car = \text{FALSE} \wedge prt = \text{TRUE}) \end{array} \right) \vee \right) \vee \left( \begin{array}{l} (prt = \text{FALSE} \wedge \\ (car = \text{TRUE} \wedge clk = \text{TRUE}) \vee \\ (car = \text{FALSE} \wedge prt = \text{TRUE}) \end{array} \right) \right)$ 
    chg := bool  $\left( \begin{array}{l} (car = \text{TRUE} \wedge clk = \text{TRUE}) \vee \\ (car = \text{FALSE} \wedge prt = \text{TRUE}) \end{array} \right)$ 
  end

```



This circuit is interesting because it contains three times the same fragment:

$$\begin{array}{l} (car = \text{TRUE} \wedge clk = \text{TRUE}) \vee \\ (car = \text{FALSE} \wedge prt = \text{TRUE}) \end{array}$$

- The previous circuit contains several occurrences of the following fragment:

$$(P \wedge Q) \vee (\neg P \wedge R)$$

  
- This will be economically represented by a special "IF-gate".
- Such a gate is pictorially represented and defined as follows:




```


priority
  when
    mode = cir
  then
    mode := env
    prt := bool  $\left( \begin{array}{l} (prt = \text{TRUE} \wedge \neg \left( \begin{array}{l} (car = \text{TRUE} \wedge clk = \text{TRUE}) \vee \\ (car = \text{FALSE} \wedge prt = \text{TRUE}) \end{array} \right) \vee \\ (prt = \text{FALSE} \wedge \left( \begin{array}{l} (car = \text{TRUE} \wedge clk = \text{TRUE}) \vee \\ (car = \text{FALSE} \wedge prt = \text{TRUE}) \end{array} \right) \end{array} \right) \vee \end{array} \right)$ 
    chg := bool  $\left( \begin{array}{l} (car = \text{TRUE} \wedge clk = \text{TRUE}) \vee \\ (car = \text{FALSE} \wedge prt = \text{TRUE}) \end{array} \right)$ 
  end


```

 


 


 
- priority on main road
- car on small road
- long delay is over



 


 


 


 


 - Priority on small road
- No cars on small road
- Long delay is not over




 

 

 

 - We connect the PRIORITY circuit to the LIGHT circuit



- We start with an abstraction of the LIGHT circuit
- It yields the colors for the main road
- The two red colors *rd1* and *rd2* are there for symmetry with *grn* and *org*

variables: *prt, grn, org, rd1, rd2*

inv0_1: *prt* ∈ BOOL

inv0_2: *grn* ∈ BOOL

inv0_3: *org* ∈ BOOL

inv0_4: *rd1* ∈ BOOL

inv0_5: *rd2* ∈ BOOL

- Always one color
- At most one color

inv0_6: $grn = \text{TRUE} \vee org = \text{TRUE} \vee rd1 = \text{TRUE} \vee rd2 = \text{TRUE}$

inv0_7: $grn = \text{TRUE} \Rightarrow org = \text{FALSE} \wedge rd1 = \text{FALSE} \wedge rd2 = \text{FALSE}$

inv0_8: $org = \text{TRUE} \Rightarrow grn = \text{FALSE} \wedge rd1 = \text{FALSE} \wedge rd2 = \text{FALSE}$

inv0_9: $rd1 = \text{TRUE} \Rightarrow grn = \text{FALSE} \wedge org = \text{FALSE} \wedge rd2 = \text{FALSE}$

inv0_10: $rd2 = \text{TRUE} \Rightarrow grn = \text{FALSE} \wedge org = \text{FALSE} \wedge rd1 = \text{FALSE}$

grn_to_org

when

mode = *cir*

prt = TRUE

grn = TRUE

then

mode := *env*

grn := FALSE

org := TRUE

end

org_to_rd1

when

mode = *cir*

org = TRUE

then

mode := *env*

org := FALSE

rd1 := TRUE

end

rd1_to_rd2

when

mode = *cir*

prt = FALSE

rd1 = TRUE

then

mode := *env*

rd1 := FALSE

rd2 := TRUE

end

rd2_to_grn

when

mode = *cir*

rd2 = TRUE

then

mode := *env*

grn := TRUE

rd2 := FALSE

end

```
grn_to_nth
  when
    mode = cir
    grn = TRUE
    prt = FALSE
  then
    mode := env
  end
```

```
rd1_to_nth
  when
    mode = cir
    rd1 = TRUE
    prt = TRUE
  then
    mode := env
  end
```

```
env_evt  
  when  
    mode = env  
  then  
    mode := cir  
    prt :∈ BOOL  
  end
```


variables: $p_{rt}, g_{rn}, o_{rg}, r_{d1}, r_{d2}$

$g_{rn_MR}, o_{rg_MR}, r_{ed_MR}$

$g_{rn_SR}, o_{rg_SR}, r_{ed_SR}$

inv1_1: $g_{rn_MR} \in \text{BOOL}$

inv1_2: $o_{rg_MR} \in \text{BOOL}$

inv1_3: $r_{ed_MR} \in \text{BOOL}$

inv1_4: $g_{rn_SR} \in \text{BOOL}$

inv1_5: $o_{rg_SR} \in \text{BOOL}$

inv1_6: $r_{ed_SR} \in \text{BOOL}$

inv1_7: $grn_MR = grn$

inv1_8: $org_MR = org$

inv1_9: $red_MR = \text{TRUE} \Leftrightarrow (rd1 = \text{TRUE} \vee rd2 = \text{TRUE})$

inv1_10: $grn_SR = rd1$

inv1_11: $org_SR = rd2$

inv1_12: $red_SR = \text{TRUE} \Leftrightarrow (grn = \text{TRUE} \vee org = \text{TRUE})$

- Lights are mutually exclusive

thm1_1: $red_MR = \text{TRUE} \Leftrightarrow (grn_SR = \text{TRUE} \vee org_SR = \text{TRUE})$

thm1_2: $red_SR = \text{TRUE} \Leftrightarrow (grn_MR = \text{TRUE} \vee org_MR = \text{TRUE})$

```
grn_to_org
  when
    mode = cir
    prt = TRUE
    grn = TRUE
  then
    mode := env
    grn := FALSE
    org := TRUE
    grn_MR := FALSE
    org_MR := TRUE
  end
```

```
org_to_rd1
  when
    mode = cir
    org = TRUE
  then
    mode := env
    org := FALSE
    rd1 := TRUE
    org_MR := FALSE
    red_MR := TRUE
    grn_SR := TRUE
    red_SR := FALSE
  end
```

```
rd1_to_rd2
  when
    mode = cir
    prt = FALSE
    rd1 = TRUE
  then
    mode := env
    rd1 := FALSE
    rd2 := TRUE
    org_SR := TRUE
    grn_SR := FALSE
  end
```

```
rd2_to_grn
  when
    mode = cir
    rd2 = TRUE
  then
    mode := env
    grn := TRUE
    rd2 := FALSE
    grn_MR := TRUE
    red_MR := FALSE
    org_SR := FALSE
    red_SR := TRUE
  end
```

```
light
  when
    mode = cir
  then
    mode := env
    grn := bool( rd2 = TRUE  $\vee$  (prt = FALSE  $\wedge$  grn = TRUE) )
    org := bool( prt = TRUE  $\wedge$  grn = TRUE )
    rd1 := bool( org = TRUE  $\vee$  (prt = TRUE  $\wedge$  rd1 = TRUE) )
    rd2 := bool( prt = FALSE  $\wedge$  rd1 = TRUE )
    grn_MR := bool( rd2 = TRUE  $\vee$  (prt = FALSE  $\wedge$  grn = TRUE) )
    org_MR := bool( prt = TRUE  $\wedge$  grn = TRUE )
    red_MR := bool( org = TRUE  $\vee$  (prt = TRUE  $\wedge$  rd1 = TRUE)  $\vee$ 
                     (prt = FALSE  $\wedge$  rd1 = TRUE) )
    grn_SR := bool( org = TRUE  $\vee$  (prt = TRUE  $\wedge$  rd1 = TRUE) )
    org_MR := bool( prt = FALSE  $\wedge$  rd1 = TRUE )
    red_MR := bool( rd2 = TRUE  $\vee$  (prt = FALSE  $\wedge$  grn = TRUE)  $\vee$ 
                     (prt = TRUE  $\wedge$  grn = TRUE) )
  end
```

